

ECGR 3183: Computer Organization - Datapath Elements

Mikey Neal

April 20, 2021

Program Counter

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Program_Counter is
  Port ( Clock : in STD_LOGIC;
        PC_INPUT : in STD_LOGIC_VECTOR (63 downto 0);
        PC_OUTPUT : out STD_LOGIC_VECTOR (63 downto 0));
end Program_Counter;

architecture Behavioral of Program_Counter is

begin
  process (Clock)
  begin
    if rising_edge(Clock) then
      PC_OUTPUT <= PC_INPUT;
    end if;
  end process;
end Behavioral;
```

Explanation

On the rising edge of the clock (denoted as “Clock”), the output (denoted as “PC_OUTPUT”) will be set equal to the current input (denoted as “PC_INPUT”).

Instruction Memory

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity INSTUCTION_RAM is
    port(write_enable, read_enable : in std_logic;
          address : in std_logic_vector(63 downto 0);
          data_in : in std_logic_vector(31 downto 0);
          data_out : out std_logic_vector(31 downto 0));
end INSTUCTION_RAM;

architecture Behavioral of INSTUCTION_RAM is

    type memory is array(0 to 255) of std_logic_vector(7 downto 0);
    signal ram : memory := (0 => "01000010",
                             1 => "00000001",
                             2 => "01000000",
                             3 => "11111000",
                             4 => "01000011",
                             5 => "10000001",
                             6 => "01000000",
                             7 => "11111000",
                             8 => "01100100",
                             9 => "00000000",
                             10 => "00000010",
                             11 => "11001011",
                             12 => "01100101",
                             13 => "00000000",
                             14 => "00000010",
                             15 => "10001011",
                             16 => "01000001",
                             17 => "00000000",
                             18 => "00000000",
                             19 => "10110100",
                             20 => "01000000",
                             21 => "00000000",
                             22 => "00000000",
                             23 => "10110100",
                             24 => "01000010",
                             25 => "00000001",
                             26 => "01000000",
                             27 => "11111000",
                             28 => "01000110",
                             29 => "00000000",
                             30 => "00000011",
                             31 => "10101010",
                             32 => "01000111",
                             33 => "00000000",
                             34 => "00000011",
                             35 => "10001010",
                             36 => "11100100",
```

```

37 => "10000000",
38 => "00000000",
39 => "11111000",
40 => "00000010",
41 => "00000000",
42 => "00000000",
43 => "00010100",
44 => "01000011",
45 => "10000001",
46 => "01000000",
47 => "11111000",
48 => "00001000",
49 => "00000000",
50 => "00000001",
51 => "10001011",
others => "00000000");

begin
  dw : process(write_enable, address, data_in) is
  begin
    if write_enable = '1' then
      ram(to_integer(unsigned(address)) + 0) <= data_in( 7 downto 0);
      ram(to_integer(unsigned(address)) + 1) <= data_in(15 downto 8);
      ram(to_integer(unsigned(address)) + 2) <= data_in(23 downto 16);
      ram(to_integer(unsigned(address)) + 3) <= data_in(31 downto 24);
    end if;
  end process dw;
  dr : process(read_enable, address) is
  begin
    if read_enable = '1' then
      data_out( 7 downto 0) <= ram(to_integer(unsigned(address)) + 0);
      data_out(15 downto 8) <= ram(to_integer(unsigned(address)) + 1);
      data_out(23 downto 16) <= ram(to_integer(unsigned(address)) + 2);
      data_out(31 downto 24) <= ram(to_integer(unsigned(address)) + 3);
    end if;
  end process dr;
end Behavioral;

```

Explanation

When the write enable (denoted as “write_enable”) is true, it will take the current input (denoted as “data_in”) and set the memory (in variable “ram”) at the address (denoted as “address”) to that value. When the read enable (denoted as “read_enable”) is true, it will take the memory (in variable “ram”) at the address (denoted as “address”) and output that value (through the signal “data_out”).

Output

 


Figure 1: Graph of the output for the Instruction Memory

Register File

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity REGISTER_FILE is
    port(write_enable : in std_logic;
          address_in, address_out_1, address_out_2 : in std_logic_vector(4 downto 0);
          data_in : in std_logic_vector(63 downto 0);
          data_out_1, data_out_2 : out std_logic_vector(63 downto 0));
end REGISTER_FILE;

architecture Behavioral of REGISTER_FILE is

    type memory is array(0 to 31) of std_logic_vector(63 downto 0);
    signal ram : memory := (
        others => "0000000000000000000000000000000000000000000000000000000000000000");
    begin
        process(write_enable, address_in, data_in, address_out_1, address_out_2) is
            begin
                if write_enable = '1' then
                    if NOT(address_in = "11111") then
                        ram(to_integer(unsigned(address_in))) <= data_in;
                    end if;
                end if;
                data_out_1 <= ram(to_integer(unsigned(address_out_1)));
                data_out_2 <= ram(to_integer(unsigned(address_out_2)));
            end process;
        end Behavioral;
    end

```

Explanation

When the write enable (denoted as “write_enable”) is true, it will take the current input (denoted as “data_in”) and set the memory (in variable “ram”) at the input address (denoted as “address_in”) to that value, unless the address is XZR, then it will do nothing. It will take the memory (in variable “ram”) at the output addresses (denoted as “address_out.1” and “address_out.2”) and output those values (through the signal “data_out_1” and “data_out_2” respective to the address_out numbers).

Output

 


Figure 2: Graph of the output for the Register File

ALU

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ALUv2 is
    Port ( A_in : in STD_LOGIC_VECTOR (63 downto 0);
          B_in : in STD_LOGIC_VECTOR (63 downto 0);
          ALU_Out : out STD_LOGIC_VECTOR (63 downto 0);
          ALU_Flags : out STD_LOGIC_VECTOR (3 downto 0);
          OPCODE : in STD_LOGIC_VECTOR (3 downto 0));
end ALUv2;
architecture Behavioral of ALUv2 is

begin
    Process (OPCODE, A_in, B_in)
        variable Temp : STD_LOGIC_VECTOR (63 downto 0);
        variable Temp_ALU_OUT : STD_LOGIC_VECTOR (63 downto 0);
        variable Temp_ALU_FLAGS : STD_LOGIC_VECTOR (3 downto 0);
        variable Temp2 : STD_LOGIC;
    begin
        ALU_Flags(0) <= '0';
        ALU_Flags(1) <= '0';
        if (OPCODE = "0010") or (OPCODE = "0110") then
            if (OPCODE = "0110") then
                Temp_ALU_FLAGS(1) := '1';
                Temp2 := '1';
                Temp := NOT(B_in);
            else
                Temp_ALU_FLAGS(1) := '0';
                Temp2 := '0';
                Temp := (B_in);
            end if;
            for i in 0 to 63 loop
                Temp_ALU_FLAGS(0) := Temp_ALU_FLAGS(1);
                Temp_ALU_OUT(i) := (Temp(i) xor A_in(i)) xor Temp_ALU_FLAGS(1);
                Temp_ALU_FLAGS(1) := (Temp(i) and A_in(i)) or
                    (Temp_ALU_FLAGS(1) and Temp(i)) or
                    (Temp_ALU_FLAGS(1) and A_in(i));
            end loop;
            ALU_Flags(0) <= Temp_ALU_FLAGS(0) xor Temp_ALU_FLAGS(1);
            ALU_Flags(1) <= Temp2 xor Temp_ALU_FLAGS(1);
        elsif (OPCODE = "0000") then
            Temp_ALU_OUT := B_in and A_in;
        elsif (OPCODE = "0001") then
            Temp_ALU_OUT := B_in or A_in;
        elsif (OPCODE = "0111") then
            Temp_ALU_OUT := B_in;
        elsif (OPCODE = "1100") then
            Temp_ALU_OUT := B_in nor A_in;
        else
    
```

```

        Temp_ALU_OUT :=
            "0000000000000000000000000000000000000000000000000000000000000000";
    end if;
    if (Temp_ALU_OUT =
        "0000000000000000000000000000000000000000000000000000000000000000") then
        ALU_Flags(2) <= '1';
    else
        ALU_Flags(2) <= '0';
    end if;
    ALU_Flags(3) <= Temp_ALU_OUT(63);
    ALU_OUT <= Temp_ALU_OUT;
end Process;
end Behavioral;

```

Explanation

The ALU takes two inputs, “A_in” and “B_in”, and acts on them based on the operation code (denoted as “OPCODE”), these codes were given in the assignment. The ALU outputs several flags in the “ALU_Flags” array, the array is formatted {Negative Flag, Zero Flag, Carry Flag, Overflow Flag}. The ALU Output is through “ALU_Out”.

Output

 


Figure 3: Graph of the output for the ALU

Data Memory

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Data_RAM is
    port(write_enable, read_enable : in std_logic;
          address, data_in : in std_logic_vector(63 downto 0);
          data_out : out std_logic_vector(63 downto 0));
end Data_RAM;

architecture Behavioral of Data_RAM is
    type memory is array(0 to 255) of std_logic_vector(7 downto 0);
    signal ram : memory := (0 => "01000010",
                             1 => "00000001",
                             2 => "01000000",
                             3 => "11111000",
                             4 => "01000011",
                             5 => "10000001",
                             6 => "01000000",
                             7 => "11111000",
                             8 => "01100100",
                             9 => "00000000",
                             10 => "00000010",
                             11 => "11001011",
                             12 => "01100101",
                             13 => "00000000",
                             14 => "00000010",
                             15 => "10001011",
                             16 => "01000001",
                             17 => "00000000",
                             18 => "00000000",
                             19 => "10110100",
                             20 => "01000000",
                             21 => "00000000",
                             22 => "00000000",
                             23 => "10110100",
                             24 => "01000010",
                             25 => "00000001",
                             26 => "01000000",
                             27 => "11111000",
                             28 => "01000110",
                             29 => "00000000",
                             30 => "00000011",
                             31 => "10101010",
                             32 => "01000111",
                             33 => "00000000",
                             34 => "00000011",
                             35 => "10001010",
                             36 => "11100100",
                             37 => "10000000",
                             38 => "00000000",
```



```

        39 => "11111000",
        40 => "00000010",
        41 => "00000000",
        42 => "00000000",
        43 => "00010100",
        44 => "01000011",
        45 => "10000001",
        46 => "01000000",
        47 => "11111000",
        48 => "00001000",
        49 => "00000000",
        50 => "00000001",
        51 => "10001011",
        others => "00000000");

begin
    dw : process(write_enable, address, data_in) is
    begin
        if write_enable = '1' then
            ram(to_integer(unsigned(address)) + 0) <= data_in( 7 downto 0);
            ram(to_integer(unsigned(address)) + 1) <= data_in(15 downto 8);
            ram(to_integer(unsigned(address)) + 2) <= data_in(23 downto 16);
            ram(to_integer(unsigned(address)) + 3) <= data_in(31 downto 24);
            ram(to_integer(unsigned(address)) + 4) <= data_in(39 downto 32);
            ram(to_integer(unsigned(address)) + 5) <= data_in(47 downto 40);
            ram(to_integer(unsigned(address)) + 6) <= data_in(55 downto 48);
            ram(to_integer(unsigned(address)) + 7) <= data_in(63 downto 56);
        end if;
    end process dw;
    dr : process(read_enable, address) is
    begin
        if read_enable = '1' then
            data_out( 7 downto 0) <= ram(to_integer(unsigned(address)) + 0);
            data_out(15 downto 8) <= ram(to_integer(unsigned(address)) + 1);
            data_out(23 downto 16) <= ram(to_integer(unsigned(address)) + 2);
            data_out(31 downto 24) <= ram(to_integer(unsigned(address)) + 3);
            data_out(39 downto 32) <= ram(to_integer(unsigned(address)) + 4);
            data_out(47 downto 40) <= ram(to_integer(unsigned(address)) + 5);
            data_out(55 downto 48) <= ram(to_integer(unsigned(address)) + 6);
            data_out(63 downto 56) <= ram(to_integer(unsigned(address)) + 7);
        end if;
    end process dr;
end Behavioral;

```

Explanation

When the write enable (denoted as “write_enable”) is true, it will take the current input (denoted as “data_in”) and set the memory (in variable “ram”) at the address (denoted as “address”) to that value. When the read enable (denoted as “read_enable”) is true, it will take the memory (in variable “ram”) at the address (denoted as “address”) and output that value (through the signal “data_out”).

Output

 


Figure 4: Graph of the output for the Data Memory

Sign Extend

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Sign_Extend is
  Port ( INST_In : in STD_LOGIC_VECTOR (31 downto 0);
        IMM_Out : out STD_LOGIC_VECTOR (63 downto 0));
end Sign_Extend;

architecture Behavioral of Sign_Extend is
begin
  process(INST_In)
  begin
    if (INST_In(31 downto 26) = "000101") then -- B
      IMM_Out(31 downto 0) <= INST_In;
      for i in 26 to 63 loop
        IMM_Out(i) <= INST_In(25);
      end loop;
    elsif (INST_In(31 downto 25) = "1011010") then -- CBZ and CBNZ
      IMM_Out(18 downto 0) <= INST_In(23 downto 5);
      for i in 19 to 63 loop
        IMM_Out(i) <= INST_In(23);
      end loop;
    elsif (INST_In(31 downto 21) = "11111000000") or
      (INST_In(31 downto 21) = "11111000010") then -- LOAD and STORE
      IMM_Out(8 downto 0) <= INST_In(20 downto 12);
      for i in 9 to 63 loop
        IMM_Out(i) <= INST_In(20);
      end loop;
    end if;
  end process;
end Behavioral;

```

Explanation

This component takes an instruction in (denoted as “INST_In”), and if it is a “B”, “CBZ”, “CBNZ”, “LDUR”, or “STUR” operation, it will extract the Immediate value, sign extend, and output to “IMM_Out”.

Output

 


Figure 5: Graph of the output for the Sign Extend