

ECGR 3183: Computer Organization - Control Units

Mikey Neal

April 27, 2021

Contents

Main Control Unit	3
VHDL Code	3
Explanation	4
Output	4
ALU Control Unit	5
VHDL Code	5
Output	5
CPU Units from the Datapath Elements Project	6
Program Counter	6
VHDL Code	6
Explanation	6
Instruction Memory	7
VHDL Code	7
Explanation	8
Output	8
Register File	9
VHDL Code	9
Explanation	9
Output	9
ALU	10
VHDL Code	10
Explanation	11
Output	11
Data Memory	12
VHDL Code	12
Explanation	13
Output	14
Sign Extend	15
VHDL Code	15
Explanation	15
Output	15

Main Control Unit

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Main_Control is
    port(
        UPPER_11_OPCODE : in std_logic_vector(10 downto 0);
        Reg2Loc : out std_logic;
        ALUSrc : out std_logic;
        MemtoReg : out std_logic;
        RegWrite : out std_logic;
        MemRead : out std_logic;
        MemWrite : out std_logic;
        Branch : out std_logic;
        UncondBranch : out std_logic;
        ALU_OP : out std_logic_vector(1 downto 0));
end Main_Control;

architecture Behavioral of Main_Control is
begin
    process (UPPER_11_OPCODE)
    begin
        if (UPPER_11_OPCODE(10 downto 5) = "000101")
            or (UPPER_11_OPCODE(10 downto 4) = "1011010") then -- CBNZ, CBZ, or B
            Reg2Loc      <= '1';
            ALUSrc       <= '0';
            --MemtoReg    <= '1';
            RegWrite     <= '0';
            MemRead      <= '0';
            MemWrite     <= '0';
            Branch       <= '1';
            UncondBranch <= NOT(UPPER_11_OPCODE(10));
            ALU_OP       <= "01";
        elsif (UPPER_11_OPCODE(10 downto 0) = "11111000000") then -- STUR
            Reg2Loc      <= '1';
            ALUSrc       <= '1';
            --MemtoReg    <= '1';
            RegWrite     <= '0';
            MemRead      <= '0';
            MemWrite     <= '1';
            Branch       <= '0';
            UncondBranch <= '0';
            ALU_OP       <= "00";
        elsif (UPPER_11_OPCODE(10 downto 0) = "11111000010") then -- LDUR
            --Reg2Loc     <= '1';
            ALUSrc       <= '1';
            MemtoReg     <= '1';
            RegWrite     <= '1';
            MemRead      <= '1';
            MemWrite     <= '0';
        end if;
    end process;
end Behavioral;

```

```

        Branch      <= '0';
        UncondBranch <= '0';
        ALU_OP      <= "00";
    else
        Reg2Loc      <= '0';
        ALUSrc       <= '0';
        MemtoReg     <= '0';
        RegWrite     <= '1';
        MemRead      <= '0';
        MemWrite     <= '0';
        Branch       <= '0';
        UncondBranch <= '0';
        ALU_OP       <= "10";
    end if;
end process;
end Behavioral;

```

Explanation

The Main Control Unit takes in the upper 11 bits of an instruction (denoted as “UPPER_11_OPCODE”) and outputs control lines for the rest of the CPU (denoted as “Reg2Loc”, “ALUSrc”, “MemtoReg”, “RegWrite”, “MemRead”, “MemWrite”, “Branch”, “UncondBranch”, and “ALU_OP”).

Output

 


Figure 1: Graph of the output for the Main Control Unit using the Instruction Memory

ALU Control Unit

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ALU_Control is
    port(
        ALU_OP : in std_logic_vector(1 downto 0);
        UPPER_11_OPCODE : in std_logic_vector(10 downto 0);
        ALU_Code : out std_logic_vector(3 downto 0));
end ALU_Control;

architecture Behavioral of ALU_Control is
begin
    process (UPPER_11_OPCODE, ALU_OP)
    begin
        if (UPPER_11_OPCODE(10 downto 0) = "10001010000") then
            ALU_Code <= "0000"; -- AND
        elsif (UPPER_11_OPCODE(10 downto 0) = "10101010000") then
            ALU_Code <= "0001"; -- ORR
        elsif (UPPER_11_OPCODE(10 downto 0) = "11111000000")
            or (UPPER_11_OPCODE(10 downto 0) = "11111000010")
            or (UPPER_11_OPCODE(10 downto 0) = "10001011000") then
            ALU_Code <= "0010"; -- STUR, LDUR, or ADD
        elsif (UPPER_11_OPCODE(10 downto 0) = "11001011000") then
            ALU_Code <= "0110"; -- SUB
        elsif (UPPER_11_OPCODE(10 downto 5) = "000101")
            or (UPPER_11_OPCODE(10 downto 4) = "1011010") then
            ALU_Code <= "0111"; -- B, CBZ, or CBNZ
        end if;
    end process;
end Behavioral;

```

Explanation

The ALU Control Unit takes in the upper 11 bits of an instruction (denoted as “UPPER_11_OPCODE”) and outputs the ALU type Operation Code (denoted as “ALU_Code”). It also takes in the “ALU_OP” from the main control, but it is unused as the “UPPER_11_OPCODE” can more easily be used to determine the instruction being used.

Output

 


Figure 2: Graph of the output for the ALU Control Unit using the Instruction Memory

CPU Units from the Datapath Elements Project

Program Counter

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Program_Counter is
  Port ( Clock : in STD_LOGIC;
        PC_INPUT : in STD_LOGIC_VECTOR (63 downto 0);
        PC_OUTPUT : out STD_LOGIC_VECTOR (63 downto 0));
end Program_Counter;

architecture Behavioral of Program_Counter is

begin
  process (Clock)
  begin
    if rising_edge(Clock) then
      PC_OUTPUT <= PC_INPUT;
    end if;
  end process;
end Behavioral;
```

Explanation

On the rising edge of the clock (denoted as “Clock”), the output (denoted as “PC.OUTPUT”) will be set equal to the current input (denoted as “PC.INPUT”).

Instruction Memory

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity INSTUCTION_RAM is
    port(write_enable, read_enable : in std_logic;
          address : in std_logic_vector(63 downto 0);
          data_in : in std_logic_vector(31 downto 0);
          data_out : out std_logic_vector(31 downto 0));
end INSTUCTION_RAM;

architecture Behavioral of INSTUCTION_RAM is

    type memory is array(0 to 255) of std_logic_vector(7 downto 0);
    signal ram : memory := (0 => "01000010",
                             1 => "00000001",
                             2 => "01000000",
                             3 => "11111000",
                             4 => "01000011",
                             5 => "10000001",
                             6 => "01000000",
                             7 => "11111000",
                             8 => "01100100",
                             9 => "00000000",
                             10 => "00000010",
                             11 => "11001011",
                             12 => "01100101",
                             13 => "00000000",
                             14 => "00000010",
                             15 => "10001011",
                             16 => "01000001",
                             17 => "00000000",
                             18 => "00000000",
                             19 => "10110100",
                             20 => "01000000",
                             21 => "00000000",
                             22 => "00000000",
                             23 => "10110100",
                             24 => "01000010",
                             25 => "00000001",
                             26 => "01000000",
                             27 => "11111000",
                             28 => "01000110",
                             29 => "00000000",
                             30 => "00000011",
                             31 => "10101010",
                             32 => "01000111",
                             33 => "00000000",
                             34 => "00000011",
```

```

35 => "10001010",
36 => "11100100",
37 => "10000000",
38 => "00000000",
39 => "11111000",
40 => "00000010",
41 => "00000000",
42 => "00000000",
43 => "00010100",
44 => "01000011",
45 => "10000001",
46 => "01000000",
47 => "11111000",
48 => "00001000",
49 => "00000000",
50 => "00000001",
51 => "10001011",
others => "00000000");

begin
  dw : process(write_enable, address, data_in) is
    begin
      if write_enable = '1' then
        ram(to_integer(unsigned(address)) + 0) <= data_in( 7 downto 0);
        ram(to_integer(unsigned(address)) + 1) <= data_in(15 downto 8);
        ram(to_integer(unsigned(address)) + 2) <= data_in(23 downto 16);
        ram(to_integer(unsigned(address)) + 3) <= data_in(31 downto 24);
      end if;
    end process dw;
  dr : process(read_enable, address) is
    begin
      if read_enable = '1' then
        data_out( 7 downto 0) <= ram(to_integer(unsigned(address)) + 0);
        data_out(15 downto 8) <= ram(to_integer(unsigned(address)) + 1);
        data_out(23 downto 16) <= ram(to_integer(unsigned(address)) + 2);
        data_out(31 downto 24) <= ram(to_integer(unsigned(address)) + 3);
      end if;
    end process dr;
end Behavioral;

```

Explanation

When the write enable (denoted as “write_enable”) is true, it will take the current input (denoted as “data_in”) and set the memory (in variable “ram”) at the address (denoted as “address”) to that value. When the read enable (denoted as “read_enable”) is true, it will take the memory (in variable “ram”) at the address (denoted as “address”) and output that value (through the signal “data_out”).

Output

 


Figure 3: Graph of the output for the Instruction Memory

Register File

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity REGISTER_FILE is
    port(write_enable : in std_logic;
          address_in, address_out_1, address_out_2 : in std_logic_vector(4 downto 0);
          data_in : in std_logic_vector(63 downto 0);
          data_out_1, data_out_2 : out std_logic_vector(63 downto 0));
end REGISTER_FILE;

architecture Behavioral of REGISTER_FILE is

    type memory is array(0 to 31) of std_logic_vector(63 downto 0);
    signal ram : memory := (
        others => "0000000000000000000000000000000000000000000000000000000000000000");
begin
    process(write_enable, address_in, data_in, address_out_1, address_out_2) is
        begin
            if write_enable = '1' then
                if NOT(address_in = "11111") then
                    ram(to_integer(unsigned(address_in))) <= data_in;
                end if;
            end if;
            data_out_1 <= ram(to_integer(unsigned(address_out_1)));
            data_out_2 <= ram(to_integer(unsigned(address_out_2)));
        end process;
    end Behavioral;

```

Explanation

When the write enable (denoted as “write_enable”) is true, it will take the current input (denoted as “data_in”) and set the memory (in variable “ram”) at the input address (denoted as “address_in”) to that value, unless the address is XZR, then it will do nothing. It will take the memory (in variable “ram”) at the output addresses (denoted as “address_out_1” and “address_out_2”) and output those values (through the signal “data_out_1” and “data_out_2” respective to the address_out numbers).

Output

 


Figure 4: Graph of the output for the Register File

ALU

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ALUv2 is
    Port ( A_in : in STD_LOGIC_VECTOR (63 downto 0);
          B_in : in STD_LOGIC_VECTOR (63 downto 0);
          ALU_Out : out STD_LOGIC_VECTOR (63 downto 0);
          ALU_Flags : out STD_LOGIC_VECTOR (3 downto 0);
          OPCODE : in STD_LOGIC_VECTOR (3 downto 0));
end ALUv2;
architecture Behavioral of ALUv2 is

begin
    Process (OPCODE, A_in, B_in)
        variable Temp : STD_LOGIC_VECTOR (63 downto 0);
        variable Temp_ALU_OUT : STD_LOGIC_VECTOR (63 downto 0);
        variable Temp_ALU_FLAGS : STD_LOGIC_VECTOR (3 downto 0);
        variable Temp2 : STD_LOGIC;
    begin
        ALU_Flags(0) <= '0';
        ALU_Flags(1) <= '0';
        if (OPCODE = "0010") or (OPCODE = "0110") then
            if (OPCODE = "0110") then
                Temp_ALU_FLAGS(1) := '1';
                Temp2 := '1';
                Temp := NOT(B_in);
            else
                Temp_ALU_FLAGS(1) := '0';
                Temp2 := '0';
                Temp := (B_in);
            end if;
            for i in 0 to 63 loop
                Temp_ALU_FLAGS(0) := Temp_ALU_FLAGS(1);
                Temp_ALU_OUT(i) := (Temp(i) xor A_in(i)) xor Temp_ALU_FLAGS(1);
                Temp_ALU_FLAGS(1) := (Temp(i) and A_in(i)) or
                    (Temp_ALU_FLAGS(1) and Temp(i)) or
                    (Temp_ALU_FLAGS(1) and A_in(i));
            end loop;
            ALU_Flags(0) <= Temp_ALU_FLAGS(0) xor Temp_ALU_FLAGS(1);
            ALU_Flags(1) <= Temp2 xor Temp_ALU_FLAGS(1);
        elsif (OPCODE = "0000") then
            Temp_ALU_OUT := B_in and A_in;
        elsif (OPCODE = "0001") then
            Temp_ALU_OUT := B_in or A_in;
        elsif (OPCODE = "0111") then
            Temp_ALU_OUT := B_in;
        elsif (OPCODE = "1100") then
    
```

```

        Temp_ALU_OUT := B_in nor A_in;
    else
        Temp_ALU_OUT :=
            "0000000000000000000000000000000000000000000000000000000000000000";
    end if;
    if (Temp_ALU_OUT =
        "0000000000000000000000000000000000000000000000000000000000000000") then
        ALU_Flags(2) <= '1';
    else
        ALU_Flags(2) <= '0';
    end if;
    ALU_Flags(3) <= Temp_ALU_OUT(63);
    ALU_OUT <= Temp_ALU_OUT;
end Process;
end Behavioral;

```

Explanation

The ALU takes two inputs, “A_in” and “B_in”, and acts on them based on the operation code (denoted as “OPCODE”), these codes were given in the assignment. The ALU outputs several flags in the “ALU_Flags” array, the array is formatted {Negative Flag, Zero Flag, Carry Flag, Overflow Flag}. The ALU Output is through “ALU_Out”.

Output

 


Figure 5: Graph of the output for the ALU

Data Memory

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Data_RAM is
    port(write_enable, read_enable : in std_logic;
          address, data_in : in std_logic_vector(63 downto 0);
          data_out : out std_logic_vector(63 downto 0));
end Data_RAM;

architecture Behavioral of Data_RAM is
    type memory is array(0 to 255) of std_logic_vector(7 downto 0);
    signal ram : memory := (0  => "01000010",
                             1  => "00000001",
                             2  => "01000000",
                             3  => "11111000",
                             4  => "01000011",
                             5  => "10000001",
                             6  => "01000000",
                             7  => "11111000",
                             8  => "01100100",
                             9  => "00000000",
                             10 => "00000010",
                             11 => "11001011",
                             12 => "01100101",
                             13 => "00000000",
                             14 => "00000010",
                             15 => "10001011",
                             16 => "01000001",
                             17 => "00000000",
                             18 => "00000000",
                             19 => "10110100",
                             20 => "01000000",
                             21 => "00000000",
                             22 => "00000000",
                             23 => "10110100",
                             24 => "01000010",
                             25 => "00000001",
                             26 => "01000000",
                             27 => "11111000",
                             28 => "01000110",
                             29 => "00000000",
                             30 => "00000011",
                             31 => "10101010",
                             32 => "01000111",
                             33 => "00000000",
                             34 => "00000011",
                             35 => "10001010",
                             36 => "11100100",
```

```


        37 => "10000000",
        38 => "00000000",
        39 => "11111000",
        40 => "00000010",
        41 => "00000000",
        42 => "00000000",
        43 => "00010100",
        44 => "01000011",
        45 => "10000001",
        46 => "01000000",
        47 => "11111000",
        48 => "00001000",
        49 => "00000000",
        50 => "00000001",
        51 => "10001011",
        others => "00000000");

begin
    dw : process(write_enable, address, data_in) is
    begin
        if write_enable = '1' then
            ram(to_integer(unsigned(address)) + 0) <= data_in( 7 downto  0);
            ram(to_integer(unsigned(address)) + 1) <= data_in(15 downto  8);
            ram(to_integer(unsigned(address)) + 2) <= data_in(23 downto 16);
            ram(to_integer(unsigned(address)) + 3) <= data_in(31 downto 24);
            ram(to_integer(unsigned(address)) + 4) <= data_in(39 downto 32);
            ram(to_integer(unsigned(address)) + 5) <= data_in(47 downto 40);
            ram(to_integer(unsigned(address)) + 6) <= data_in(55 downto 48);
            ram(to_integer(unsigned(address)) + 7) <= data_in(63 downto 56);
        end if;
    end process dw;
    dr : process(read_enable, address) is
    begin
        if read_enable = '1' then
            data_out( 7 downto  0) <= ram(to_integer(unsigned(address)) + 0);
            data_out(15 downto  8) <= ram(to_integer(unsigned(address)) + 1);
            data_out(23 downto 16) <= ram(to_integer(unsigned(address)) + 2);
            data_out(31 downto 24) <= ram(to_integer(unsigned(address)) + 3);
            data_out(39 downto 32) <= ram(to_integer(unsigned(address)) + 4);
            data_out(47 downto 40) <= ram(to_integer(unsigned(address)) + 5);
            data_out(55 downto 48) <= ram(to_integer(unsigned(address)) + 6);
            data_out(63 downto 56) <= ram(to_integer(unsigned(address)) + 7);
        end if;
    end process dr;
end Behavioral;

```

Explanation

When the write enable (denoted as “write_enable”) is true, it will take the current input (denoted as “data_in”) and set the memory (in variable “ram”) at the address (denoted as “address”) to that value. When the read enable (denoted as “read_enable”) is true, it will take the memory (in variable “ram”) at the address (denoted as “address”) and output that value (through the signal “data_out”).

 Output**Figure 6: Graph of the output for the Data Memory**

Sign Extend

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Sign_Extend is
    Port ( INST_In : in STD_LOGIC_VECTOR (31 downto 0);
          IMM_Out : out STD_LOGIC_VECTOR (63 downto 0));
end Sign_Extend;

architecture Behavioral of Sign_Extend is
begin
    process(INST_In)
    begin
        if (INST_In(31 downto 26) = "000101") then -- B
            IMM_Out(31 downto 0) <= INST_In;
            for i in 26 to 63 loop
                IMM_Out(i) <= INST_In(25);
            end loop;
        elsif (INST_In(31 downto 25) = "1011010") then -- CBZ and CBNZ
            IMM_Out(18 downto 0) <= INST_In(23 downto 5);
            for i in 19 to 63 loop
                IMM_Out(i) <= INST_In(23);
            end loop;
        elsif (INST_In(31 downto 21) = "11111000000") or
              (INST_In(31 downto 21) = "11111000010") then -- LOAD and STORE
            IMM_Out(8 downto 0) <= INST_In(20 downto 12);
            for i in 9 to 63 loop
                IMM_Out(i) <= INST_In(20);
            end loop;
        end if;
    end process;
end Behavioral;

```

Explanation

This component takes an instruction in (denoted as “INST_In”), and if it is a “B”, “CBZ”, “CBNZ”, “LDUR”, or “STUR” operation, it will extract the Immediate value, sign extend, and output to “IMM_Out”.

Output

 


Figure 7: Graph of the output for the Sign Extend